

(1)

$$F(s) = \frac{s \left(\frac{s}{\omega_3} \pm 1 \right)^L K}{\left(\frac{s}{\omega_1} + 1 \right) \left(\frac{s}{\omega_2} + 1 \right)^2}$$

$$F(\omega) \Big|_{\omega_1 < \omega < \omega_2} = \frac{\pm \omega}{\omega_1} K = \pm A \Rightarrow K = \pm \frac{A}{\omega_1}$$

$$F(s) = \frac{\pm A}{\omega_1} \frac{\left(\frac{s}{\omega_3} \pm 1 \right)^L s}{\left(\frac{s}{\omega_1} + 1 \right) \left(\frac{s}{\omega_2} + 1 \right)^2}$$

(2)

$$1. \quad (V_0 - V_1) \cdot sC_1 + g_m V_1 + g_0 V_0 + sC_0 V_0 = 0$$

$$V_0 (sC_1 + sC_0 + g_0) = V_1 (sC_1 - g_m)$$

$$\frac{V_0}{V_1} = \frac{sC_1 - g_m}{s(C_1 + C_0) + g_0}$$

2.

$$V_0(t) = A \frac{j\omega_0 C_1 - g_m}{j\omega_0 (C_1 + C_0) + g_0} \cdot \sin(\omega_0 t + \varphi) \quad (A)$$

$$\frac{j\omega_0 C_1 - g_m}{j\omega_0 (C_1 + C_0) + g_0} = \frac{(j\omega_0 C_1 - g_m) (g_0 - j\omega_0 (C_1 + C_0))}{g_0^2 + \omega_0^2 (C_1 + C_0)^2} =$$

$$\frac{j\omega_0 C_1 g_0 + g_m j\omega_0 (C_1 + C_0) - g_0 g_m + \omega_0^2 (C_1 + C_0) C_1}{g_0^2 + \omega_0^2 (C_1 + C_0)^2}$$

$$\varphi = \arctg \left[\frac{\omega_0 (C_1 g_0 + g_0 m (C_1 + C_0))}{\omega_0^2 (C_1 + C_0) C_1 - g_0^2} \right]$$

3.

$$v_0(s) = V_1(s) \cdot \frac{sC_1 - j^m}{s(C_1 + C_0) + g_0} = \frac{A \omega_0}{s^2 + \omega_0^2} \cdot \frac{sC_1 - j^m}{s(C_1 + C_0) + g_0} =$$

$$\frac{K_1}{s(C_1 + C_0) + g_0} + \frac{K_2}{s + j\omega_0} + \frac{K_2^*}{s - j\omega_0}$$

due o regime permanente


Transitorio

$$K_1 = \frac{A \omega_0}{s^2 + \omega_0^2} (sC_1 - j^m) \Big|_{s = -\frac{g_0}{C_1 + C_0}} = -\frac{A \omega_0}{\left(\frac{g_0}{C_1 + C_0}\right)^2 + \omega_0^2} \left(\frac{g_0 C_1}{C_1 + C_0} - j^m\right)$$

Transitorio

$$\mathcal{L}^{-1} \left(\frac{K_1}{s(C_1 + C_0) + g_0} \right) = \mathcal{L}^{-1} \left(\frac{K_1}{(C_1 + C_0) \left(s + \frac{g_0}{C_1 + C_0} \right)} \right) = \left(\frac{K_1}{C_1 + C_0} \right) e^{-\frac{g_0}{C_1 + C_0} t} \quad (B)$$

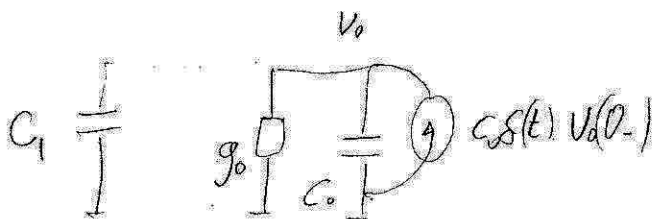(4) Para condição inicial consideramos a fonte de corrente




SOMA-SE

$$(A) + (B) + (C)$$

$$v_0 (sC_1 + sC_0) + v_0 g_0 = C_0 v_0(0-)$$

$$v_0 = \frac{C_0 v_0(0-)}{s(C_1 + C_0) + g_0} \Rightarrow v_0(t) = \frac{C_0 v_0(0-)}{C_1 + C_0} e^{-\frac{g_0}{C_1 + C_0} t} \quad (C)$$

3

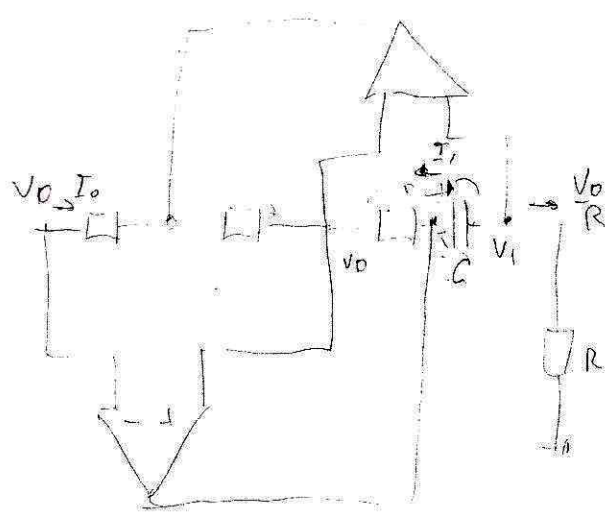

$$V_0 = R_1 I_1$$


$$= V_0 - \frac{V_0 R_1}{R^2 SC}$$

$$= V_1 + \frac{V_0}{R^2 SC}$$

$$I_1 = \left(V_0 + \frac{V_0}{R^2 SC} - V_0 \right) \frac{1}{R} = \frac{V_0}{R^2 SC}$$


$$I_0 = \left(V_0 - V_0 + \frac{V_0 R_1}{R^2 SC} \right) \frac{1}{R_1} = \frac{V_0}{R^2 SC}$$

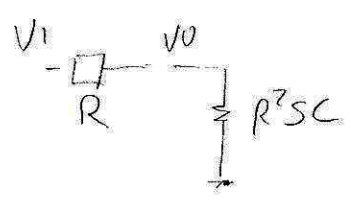
$$\left(\frac{V_0}{I_0} = R^2 SC \right)$$





$$V_0 = \frac{R^2 SC}{R + R^2 SC} = \frac{R^2 SC}{1 + R^2 SC}$$

MODULO

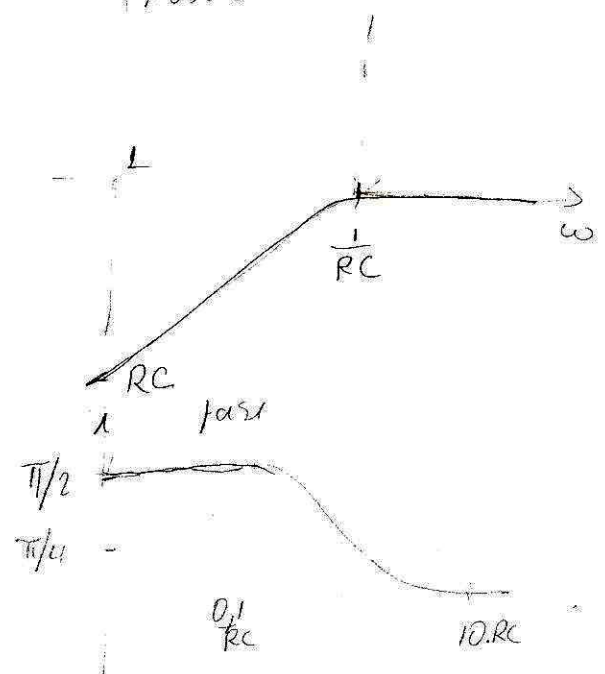

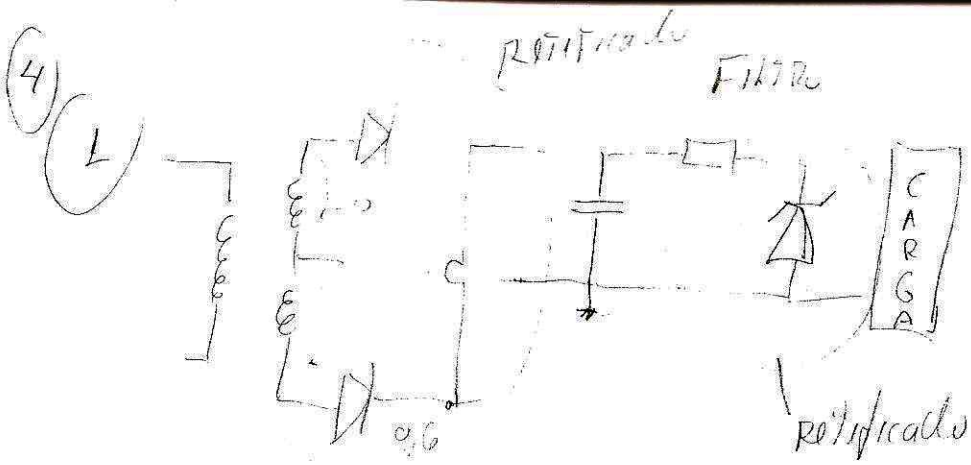


2

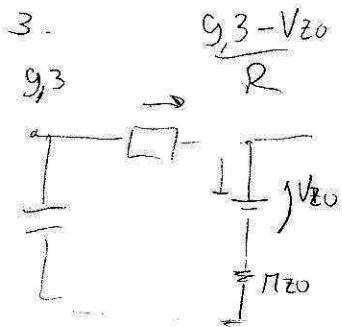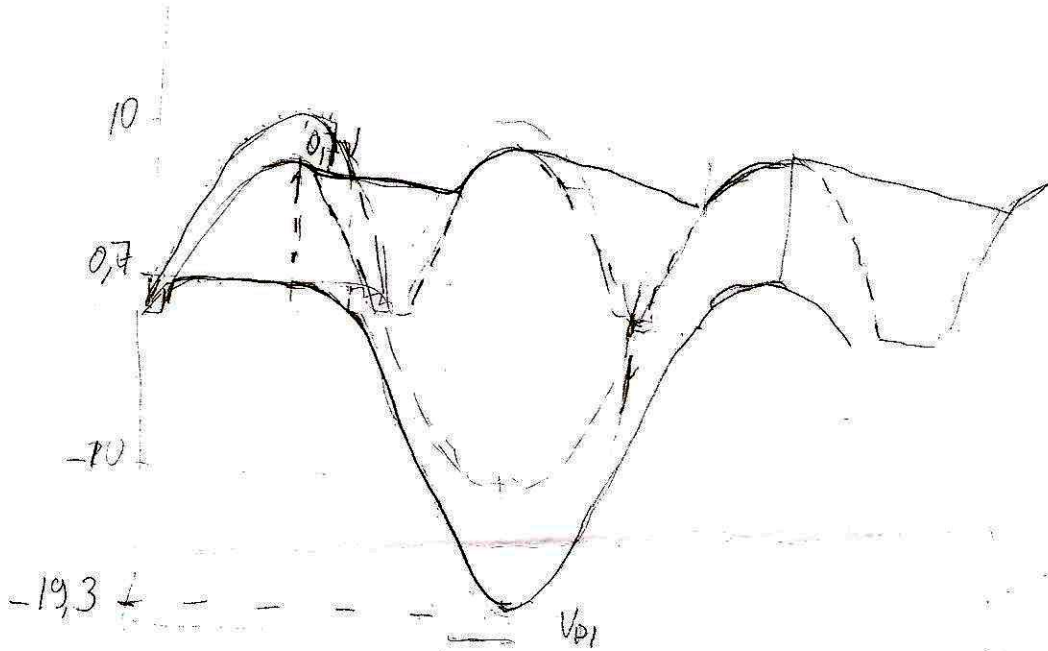


$$\Delta V \cdot C = I \cdot \frac{T}{2} = \left(\frac{9,3 - V_{zo}}{R} \right) \cdot \frac{2\pi}{\omega} \Rightarrow$$
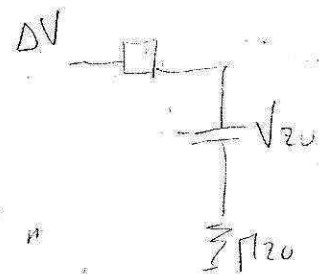
$$\Delta V = \frac{(9,3 - V_{zo}) \cdot \pi}{RC \omega}$$



$$\Delta V_o = \left(\frac{\Delta V}{R + r_{Lz}} \right) \cdot r_{Lz}$$

(9,3-0)

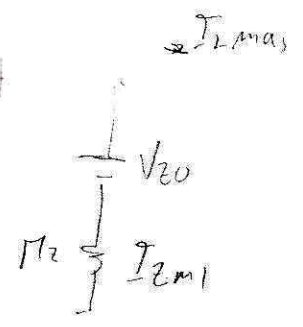

$$\frac{9,2 - (V_{20} + I_{2min} R_2)}{R} \geq I_{2max} + I_{2min}$$

$$R \leq \frac{9,2 - (V_{20} + I_{2min} R_2)}{I_{2max} + I_{2min}}$$

